

ESD


FPPA2000 ESD Protection developed along Intersil guidelines
Goal is 1500V HBM, satisfying **zap** between *any* two pads

Design kit incorporates special protection diodes
Transient clamps have been added


Analog inputs have additional protection in order to avoid
breakdown or excessive current



 Power Connections - Chip and Circuit Card



ESD Configuration

 

ESD Detail (I.)

All pins have ESD diodes to V+ and V- ***except*** for the two sensitive inputs

VCC_PA is ESD diode clamped to VCC


VEE_PA is ESD diode clamped to VEE

VCC_O is ESD diode clamped to VCC_D

VEE_O is ESD diode clamped to VEE_O


① Normal I/O pin

② Sensitive Input - special protection

 

Photodetector (External to chip)

ESD Detail (II.) Voltage Limits

 

	Zap $1 \leftrightarrow 2$	Zap $1 \leftrightarrow 3$	Zap $1 \leftrightarrow 8$
①	$5 + V_D$	$5 + V_D$	$5 + V_D$
②	$6 - V_D$	0	0
③	0	$8 - V_D$	0
④	0	0	0
⑤	$7 + V_D$	$7 + V_D$	$7 + V_D$
⑥	$8 - V_D$	$8 + V_D$	$8 + V_D$
⑦	$8 + V_C$	$8 + V_C$	$8 + V_C$
⑧	$-V_C/2$	$-(V_C + V_D)/2$	$-(V_C + 2V_D)/2$

Voltages at nodes during ZAP!

Seems ok.

V_D is one diode drop
 V_C is the voltage across the supply clamp




Goal: avoid coupling noise (esp. V_{CC}/V_{EE}) into preamp input

Preamplifier Input - ESD

- ② diodes to V+
- ② diodes to V-

Preamp
Input

Input PNP
B-C diode

 

Sets baseline
take advantage of
external C to reduce
coupling via diode

Large input PNP

Copy of large input PNP

Base current comp.




Sensitive Differential Pair Input

Photodetector leakage current measurement


Want error ≤ 20 nA.

 Concern is radiation-induced leakage current in ESD diodes
(but tests indicate that this actually works fine \rightarrow)




Irradiation Results

 FPPA2000 irradiation at LBL 88" cyclotron
Sensitivity of circuit $\sim 0.5 \text{ nA/LHC_year}$ (i.e. no problem)




ESD Diode Rules


2kV HBM

 



100 pF
IC = 2kV

 

 $V_{PEAK} = 12\text{Volts}/N$
for N diodes in parallel
To limit to 3V, use at least 4 diodes



Supply Clamps

  

Transient clamps from V_{CC} to V_{EE} (analog and digital)

No diode clamp between analog and digital V_{CC} (Power supply startup)

(zaps between V_{CC} pins clamped via V_{EE} diodes and one transient clamp)

Analog V_{EE} (-2V) diode clamped to Digital V_{EE} (0V)

EPI tie pad diode clamped to (digital) 0V

