

Introduction



Adam Davis

Electronics System Support


Layout of Talk



- What is the TCM?
- Problems with the TCM
- Status of the TCM
- Decisions we made
- Where we are now
- Further testing problems
- Future ALC Designs Considerations

What is the TCM

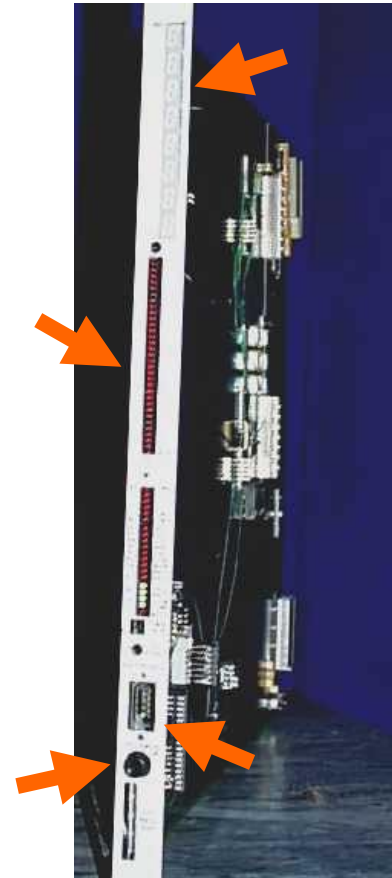- 9U Module
- VME Hex Display
- VME LED Display
- TTC
- CAN Bus





Problems with the TCM



- Connector
 - Incorrect wiring (Write*)
- VME Decoder
 - Net Names
 - Firmware(addrdec)
- Register Decoder
 - Net Names
 - Firmware(en2reg)
- Dual Port Memory
 - Net names
 - Timing problems
- Hex Display
 - Firmware
 - Timing problems

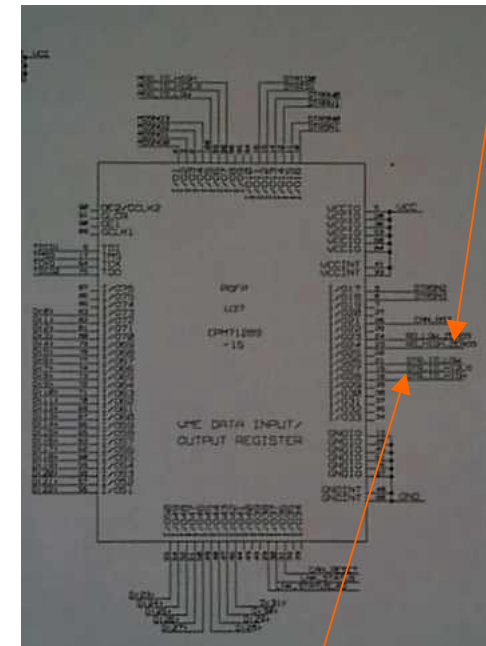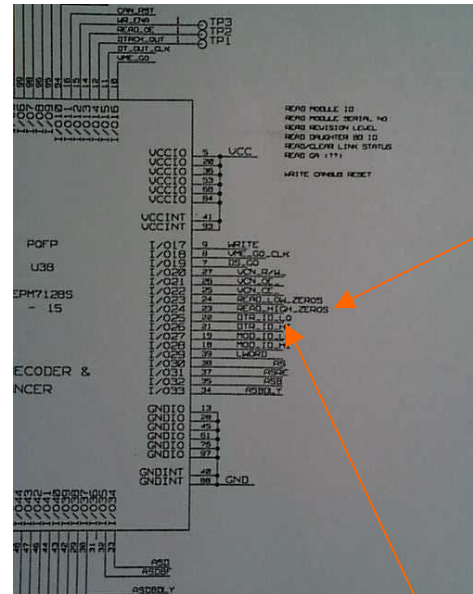
Problem with the TCM

- Schematic
- READ_HIGH_ZEROS
- RD_HIGH_ZEROS
- DTR_ID_HI
- DTR_ID_HIGH




Problems with the TCM

- Nets mixed up
 - VCN_R/W
 - VCN_OE_

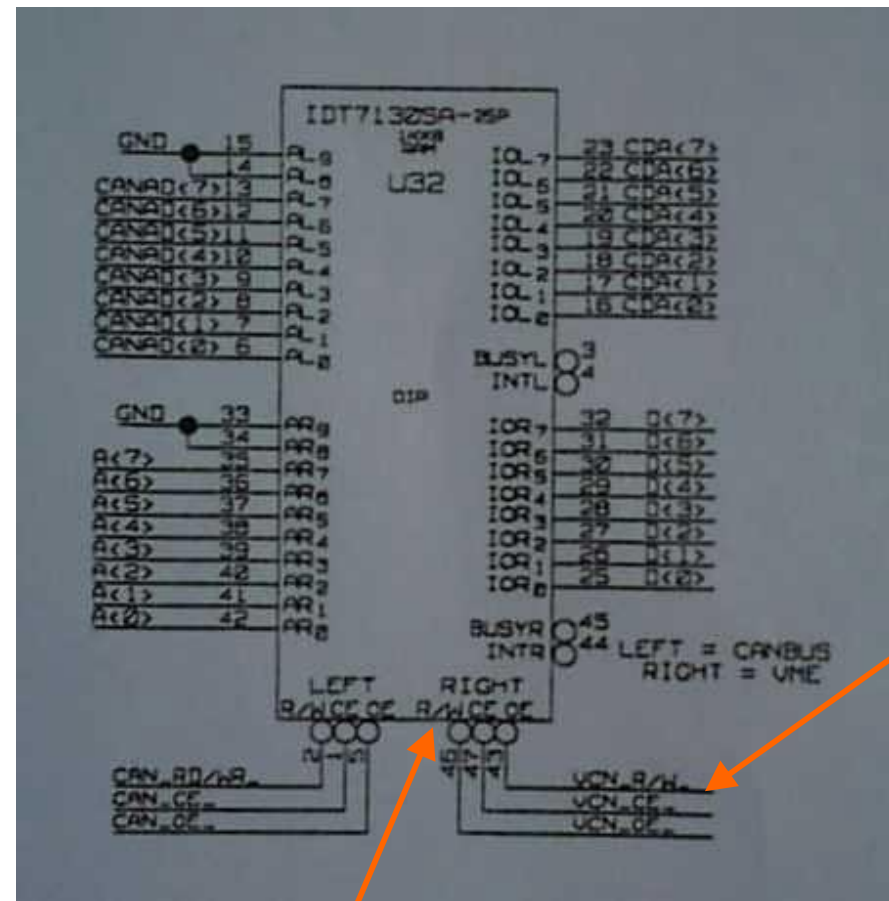

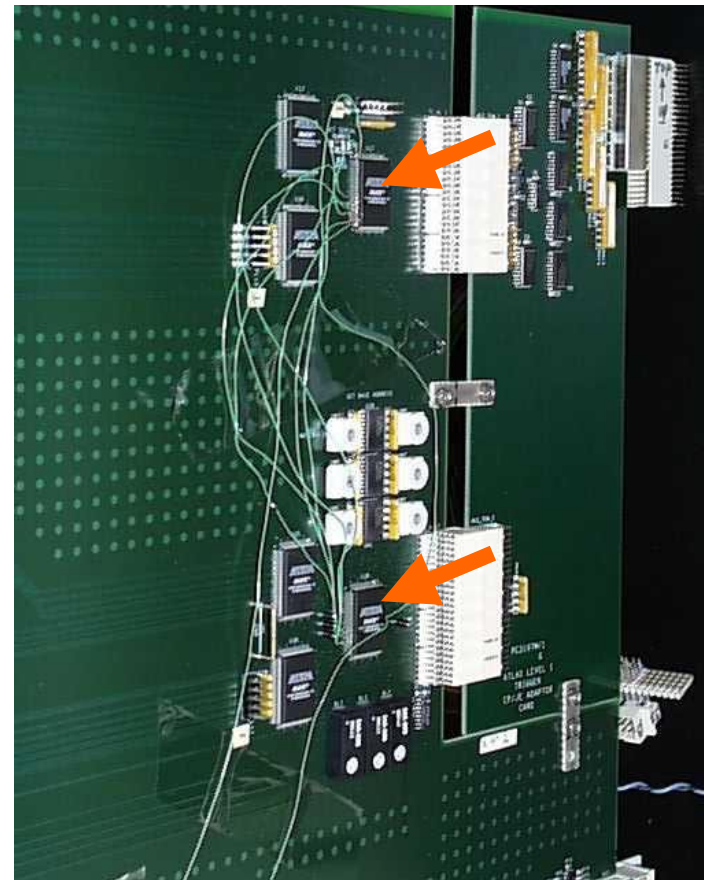Problems with the TCM

- 9 Wire Modifications
- VME Decoder
- Register Decoder




Problems with the TCM




- Could these errors been avoided.?
 - Check schematic
 - Check net list
 - Check again
 - Is there a way of checking the net list automatically.? Yes there is...

Problems with the TCM

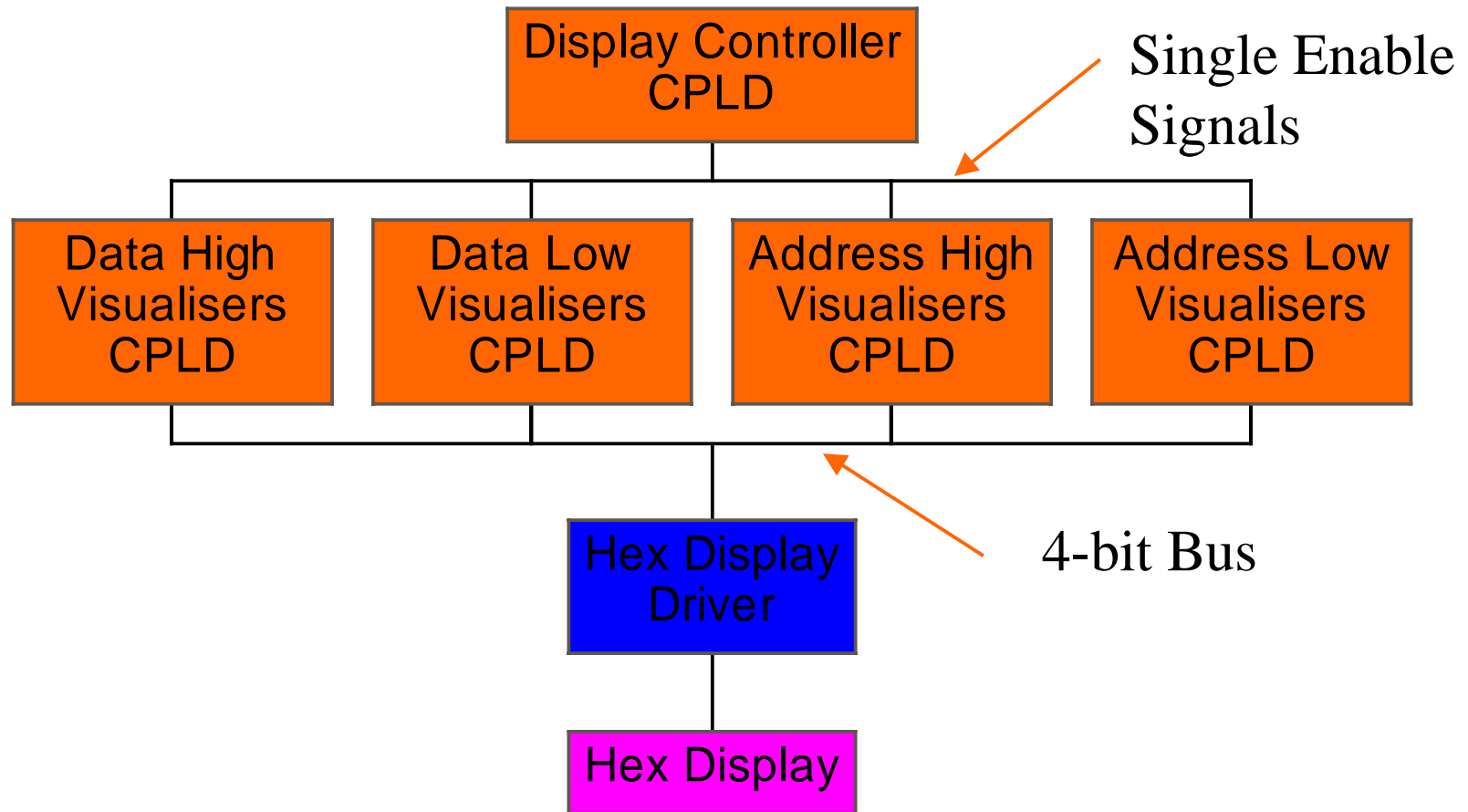

Problems with the TCM

Tri_state buffer

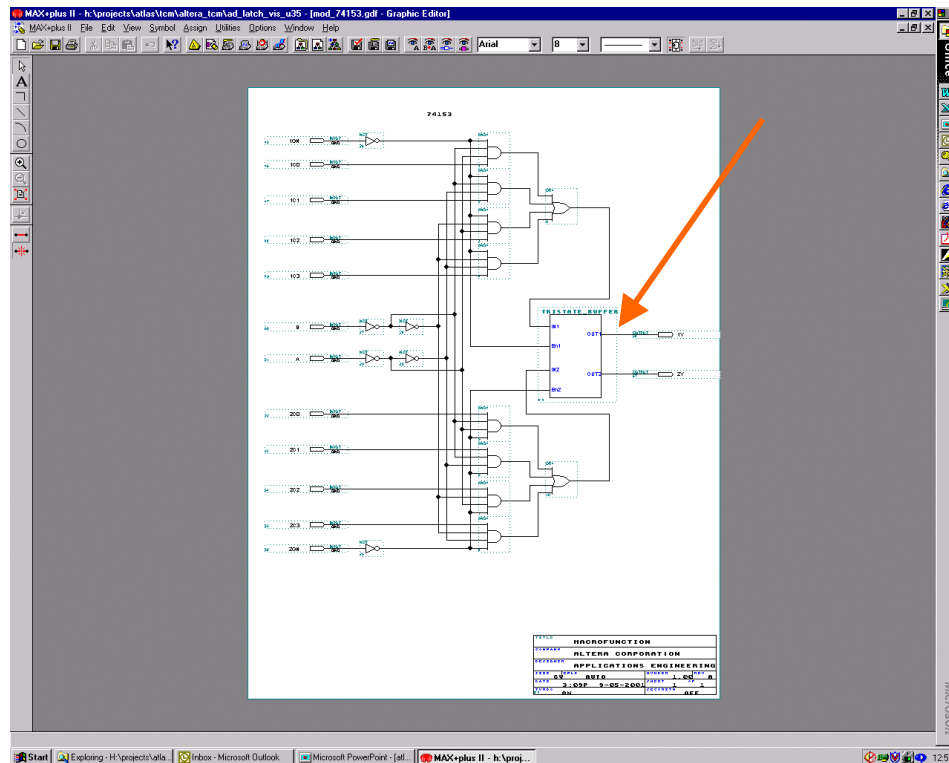

```
TITLE "tristate_buffer";

SUBDESIGN tristate_buffer
(
    IN1, IN2, En1, En2           :INPUT;
    OUT1, OUT2                  :BIDIR;
)

VARIABLE
    OUT1_TNODE, OUT2_TNODE     :TRI_STATE_NODE;

BEGIN

    OUT1_TNODE = TRI(IN1, En1);
    OUT1 = OUT1_TNODE;

    OUT2_TNODE = TRI(IN2, En2);
    OUT2 = OUT2_TNODE;

END;
```

Status of the TCM



- Read Module ID Code "3195"
- Read Module Serial Number
- Read Daughter Serial Number
- CAN Micro controller Reset


Status of the TCM



- Write to DPM
- Read from DPM
- “Hex display” display’s Address
- “Hex display” display’s Data
- LED’s Display correct Data + Address

Decisions

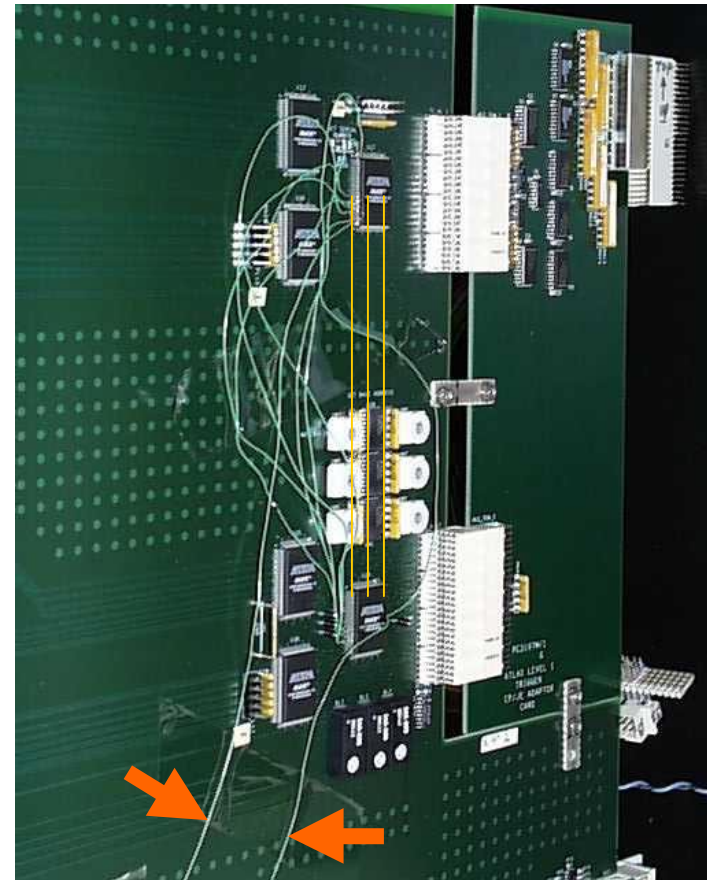- Do we need to make these modifications?
- Yes, but only two of them (link status)
- Use three enable signals for address decoding and eliminate 7 wire modifications.



Decisions



- Or, we could make the boards again taking into account the required modifications but keeping the original(ish) CPLD design.

Decisions



■ Change CPLD Design

- Keep and use boards already made(7) - 3 populated
- New boards will have more recourses, allowing for expansion of design

■ Modify Boards

- Don't spend time modifying CPLD design
- Easier to debug
- Using design to full extent and as it was originally intended

Decisions



- Recommendations
- Redesign the CPLD's
- 6 boards only need wire 2 modifications
- New boards with modifications increasing recourses if necessary


```
MAX+plus II - h:\projects\atlas\atlas\altera_tcm\rd_wr_strobes_mod - [rd_wr_strobes_mod.tdf - Text Editor]
MAX+plus II File Edit Templates Assign Utilities Options Window Help
Fixedsys 10

TITLE "Read Write Strobes";

SUBDESIGN rd_wr_strobes_mod
(
  read, write, lword      : INPUT;
  a[7..0]                 : INPUT;
  addr_ok                 : INPUT;

  mod_id_lo, mod_id_hi    : BIDIR;
  mod_id_hi2lo           : OUTPUT;

  dtr_id_lo, dtr_id_hi    : BIDIR;
  dtr_id_hi2lo           : OUTPUT;
  read_high_zeros, read_low_zeros : BIDIR;

  lnk_status              : BIDIR;
  can_rst                 : OUTPUT;

  dpmem_en_              : OUTPUT;
)
BEGIN
DEFAULTS
  dpmem_en_ = UCC;
END DEFAULTS;
mod_id_lo = TRI(0,GND);
mod_id_hi = TRI(0,GND);
dtr_id_lo = TRI(0,GND);
dtr_id_hi = TRI(0,GND);
read_high_zeros = TRI(0,GND);
read_low_zeros = TRI(0,GND);
lnk_status = TRI(0,GND);
TABLE
addr_ok, read, a[7..0] => dtr_id_hi2lo, mod_id_hi2lo, can_rst;
1,1,B"00000000" => 0,0,1;
1,1,B"00000010" => 0,1,0;
1,1,B"00000100" => 0,1,1;
1,1,B"00000110" => 1,0,0;
1,1,B"00001000" => 1,0,1;
1,0,B"00001010" => 1,1,0;
1,1,B"00001100" => 1,1,1;
0,x,B"xxxxxxx" => 0,0,0;
END TABLE;
TABLE
addr_ok, a[7..0] => dpmem_en_;
1, B"001xxxxx" => 0;
1, B"01xxxxxx" => 0;
END TABLE;
END;
```

MAX+plus II - h:\projects\atlas\tcm\altera_tcm\rd_wr_strobes_mod - [rd_wr_strobes_mod.scf - Waveform Editor]

MAX+plus II File Edit View Node Assign Utilities Options Window Help

Ref: 0.0ns Time: 0.0ns Interval: 0.0ns

0.0ns 20.0ns 40.0ns 60.0ns 80.0ns 100.0ns 120.0ns 140.0ns 160.0ns 180.0ns 200.0ns 220.0ns 240.0ns 260.0ns

Name:	Value:
read	0
addr_ok	0
a[7..0]	H 00 00 01 02 03 04 05 06 07 08 09 0A 0B 0C 0D 0E 0F 00 01 02 03 04 05 06
dtr_id_hi2lo	0
mod_id_hi2lo	0
can_rst	0
ad_low_zeros	Z
ad_high_zeros	Z
mod_id_lo	Z
mod_id_hi	Z
lnk_status	Z
dtr_id_lo	Z
dtr_id_hi	Z
dpmem_en_	1

Office

Microsoft

Start Inbox - Microsoft Outlook Microsoft PowerPoint - [atl... Microsoft Photo Editor - [e... Eidos Interactive UK - Com... MAX+plus II - h:\proj... 10:49

MAX+plus II - h:\projects\atlas\atcm\altera_tcm\rd_wr_strobes_mod - [rd_wr_strobes_mod.scf - Waveform Editor]

MAX+plus II File Edit View Node Assign Utilities Options Window Help

Ref: 240.0ns Time: 442.3ns Interval: 202.3ns

Name:	Value:	460.0ns	480.0ns	500.0ns	520.0ns	540.0ns	560.0ns	580.0ns	600.0ns	620.0ns	640.0ns	660.0ns	680.0ns	700.0ns	720.0ns														
read	1	[High]																											
addr_ok	0	[Low]																											
a[7..0]	H 04	08	09	0A	0B	0C	0D	0E	0F	10	11	12	13	14	15	16	17	18	19	1A	1B	1C	1D	1E	1F	20	21	22	23
dtr_id_hi2lo	0	[Low]																											
mod_id_hi2lo	0	[Low]																											
can_rst	0	[Low]																											
ad_low_zeros	Z	[Z]																											
ad_high_zeros	Z	[Z]																											
mod_id_lo	Z	[Z]																											
mod_id_hi	Z	[Z]																											
lnk_status	Z	[Z]																											
dtr_id_lo	Z	[Z]																											
dtr_id_hi	Z	[Z]																											
dpmem_en_	1	[Low]																											


Office

Microsoft



Start | Inbox - Microsoft Outlook | Microsoft PowerPoint - [atl... | Microsoft Photo Editor - [e... | Eidos Interactive UK - Com... | MAX+plus II - h:\proj... | 10:54

Now where are we.?

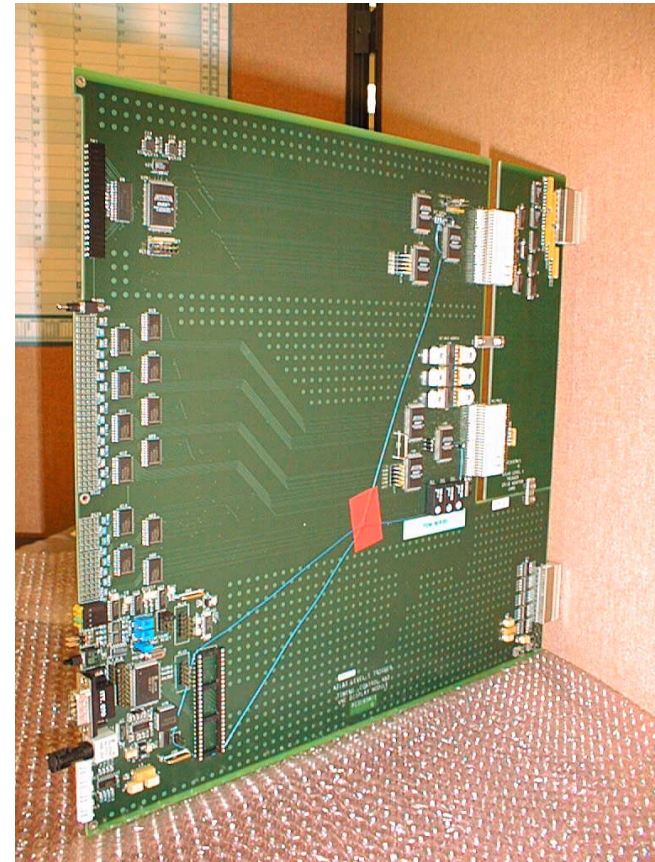- Binary decoded addressing has been implemented and all registers work OK.
- Takes only 1 - 2 hours to modify and program CPLD's.




The Improvement

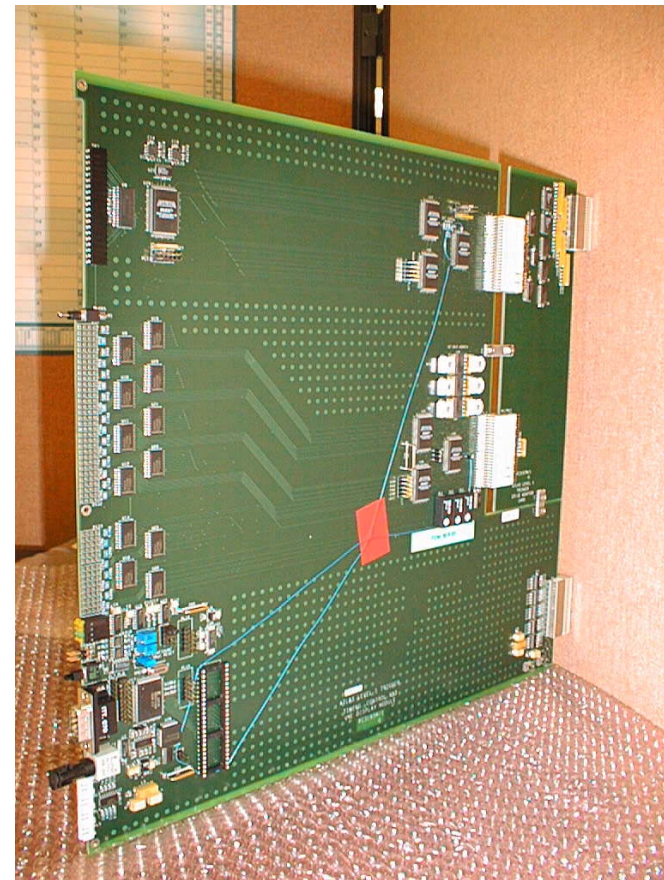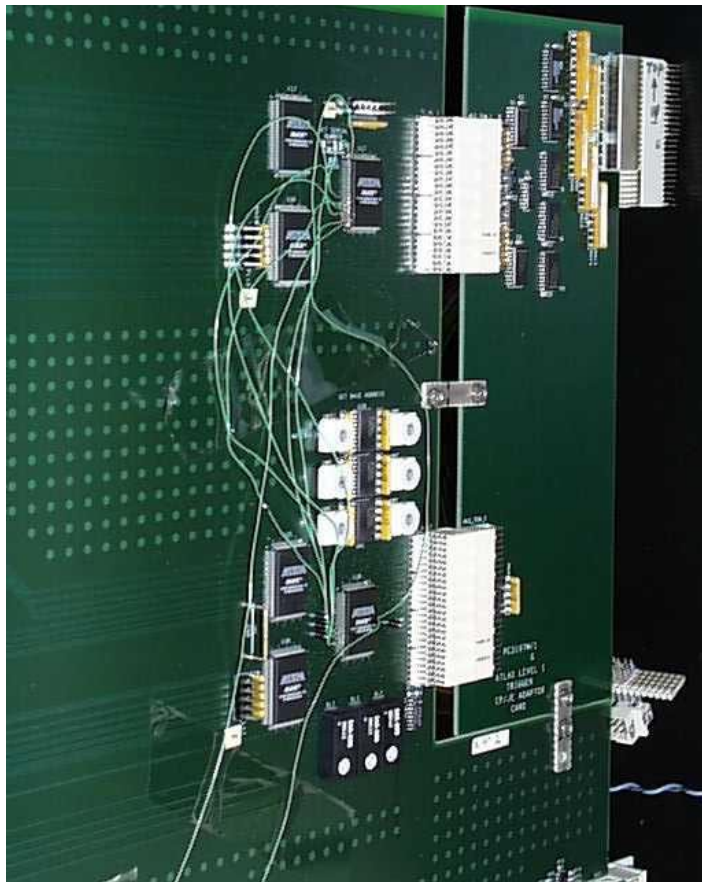

Further Testing Problems

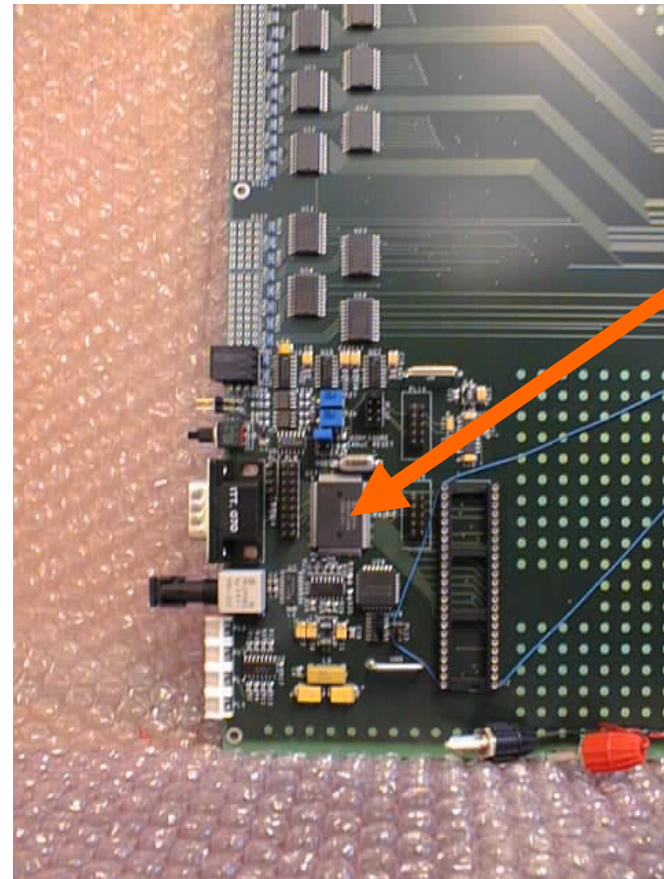- Can not download to the CAN micro on the "old board".
- New board can obtain connection, continue tests with new board, maybe.!




Further Testing Problems



- Microprocessor responds correctly to serial commands.
- MAX232 was found to be dead, not giving output.
- Capacitors C27 and C25 were placed on the schematic the wrong. Pulling down internally generated voltage supply.


Further Testing Problems

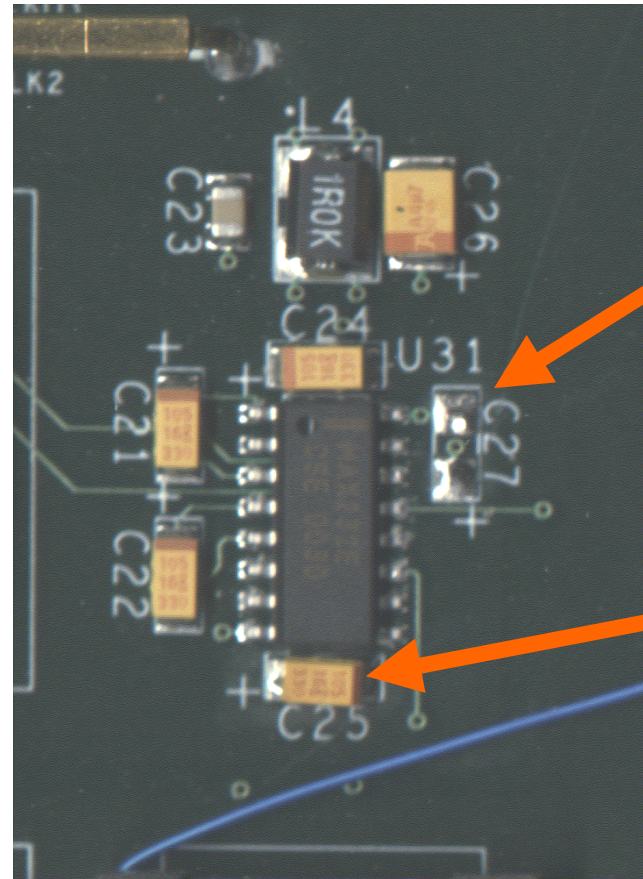- Capacitors around the wrong way.!
- C27 de-couple +5V on board. Bang.!!
- C25 de-couple internal 232 supply.




Future ALC Designs

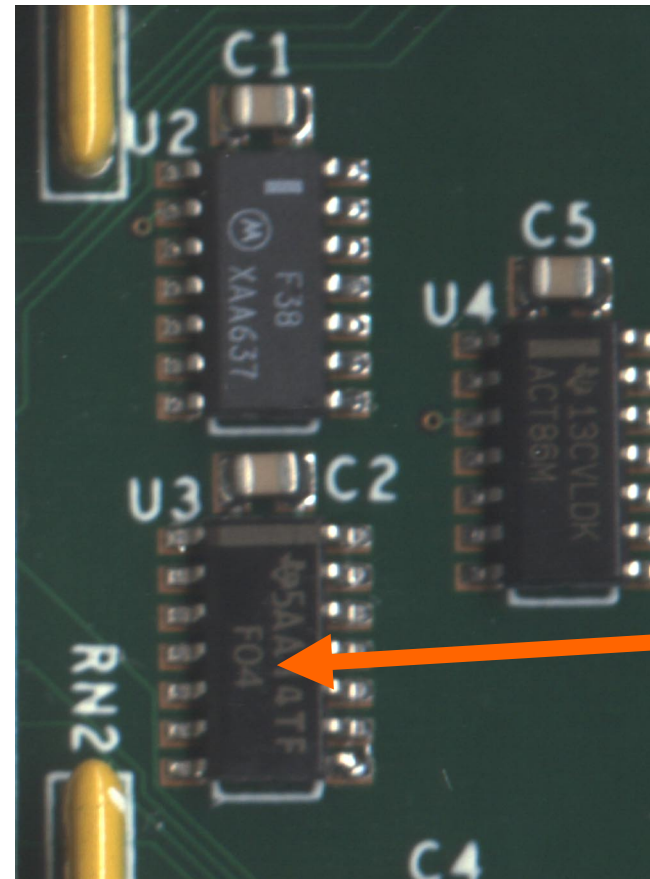- No Need for U3 to feed back DTACK signal.
- It is generated on-board.!



ALC Design Considerations

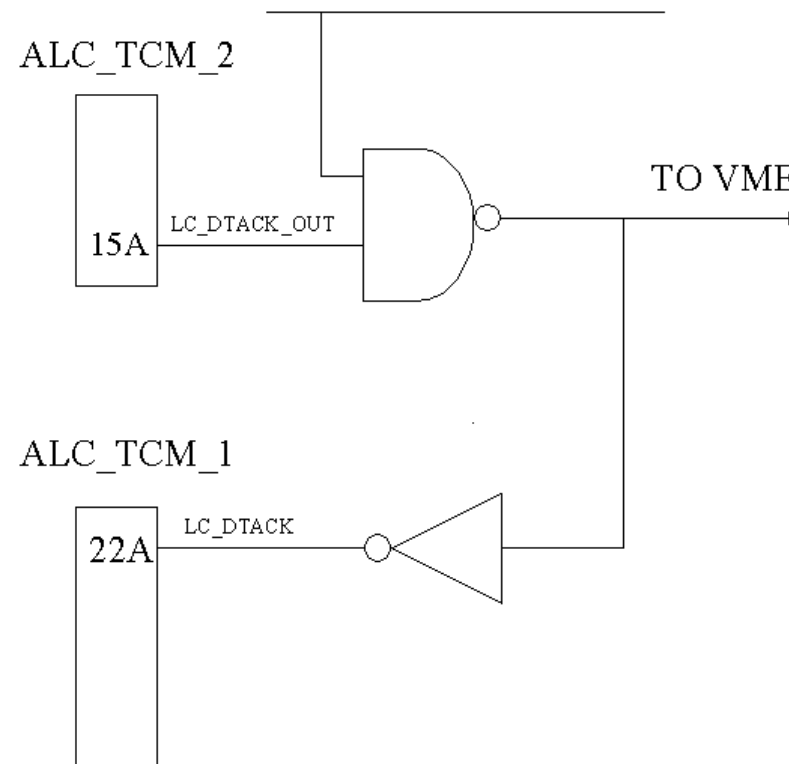- Circuit not required.
- No need to feed signal back to ALC_TCM_1.
- DTACK is generated on board.



Finally



- PECL Distribution, OK.
- CAN Buss download, OK

- Left to test:-
 - CAN controller.
 - Works in the new crate.

Time Scales



- Do We get the other boards populated?
- CAN Buss Interface working?
- ???????