#### Introduction


Adam Davis Electronics System Support

# Layout of Talk

- What is the TCM?
- Problems with the TCM
- Current Status of the TCM
- Future Options
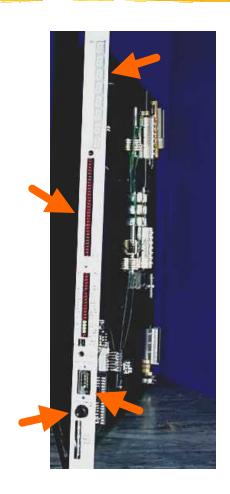
#### What is the TCM


- 9U Module
- VME Hex Display
- VME LED Display
- TTC
- **CAN Bus**




- Connector
  - Incorrect wiring (Write\*)
- VME Decoder
  - Net Names
  - Firmware(adddec)
- Register Decoder
  - Net Names
  - Firmware(en2reg)


- Dual Port Memory
  - Net names
  - Timing problems
- Hex Display
  - Firmware
  - Timing problems

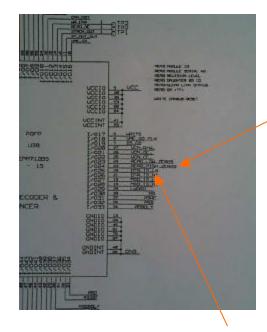- Schematic
- READ\_HIGH\_ZEROS
- RD\_HIGH\_ZEROS
- DTR\_ID\_HI
- DTR\_ID\_HIGH




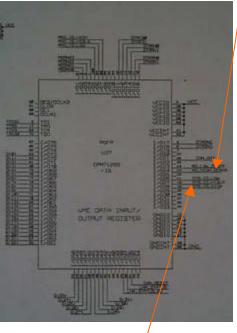

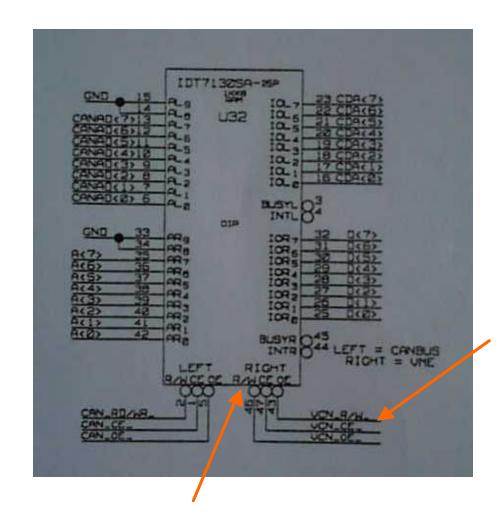
- Nets mixed up
  - VCN\_R/W
  - VCN\_OE\_



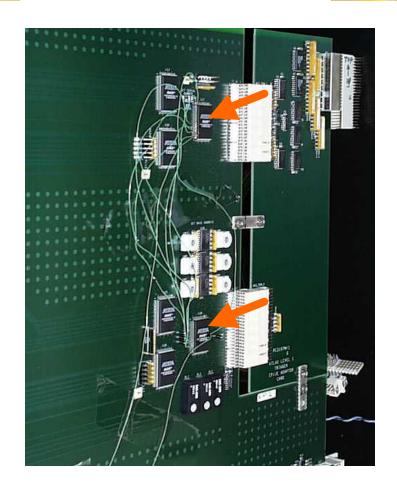
- 9 Wire Modifications
- VME Decoder
- Register Decoder



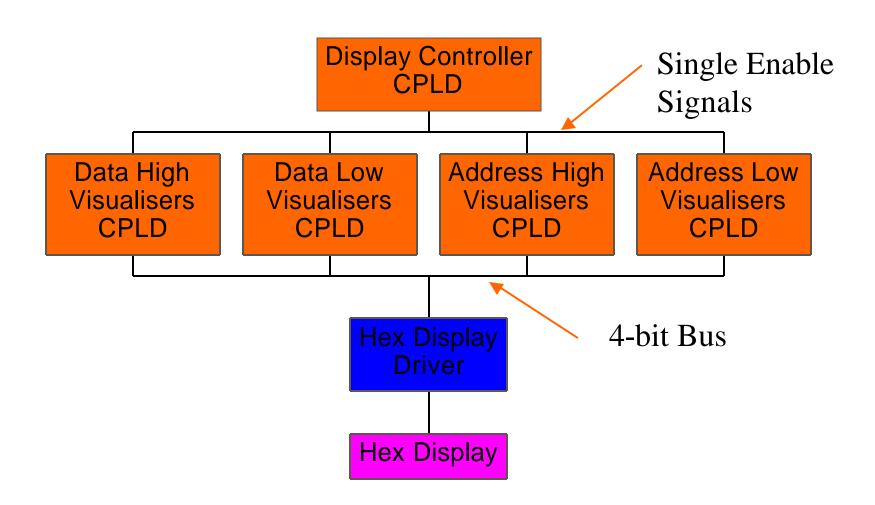- Could these errors been avoided.?
- Check schematic
- Check net list
- Check again
- Is there a way of checking the net list automatically.?



Tri\_state buffer

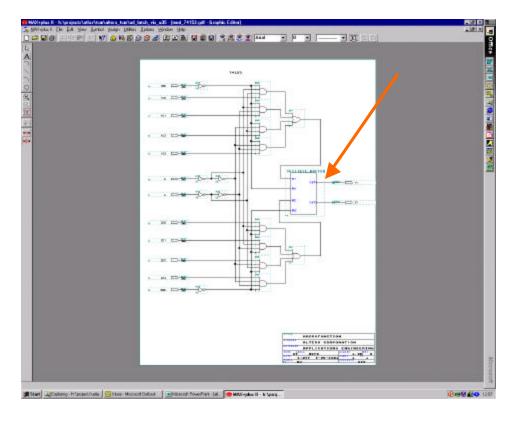

```
TITLE "tristate_buffer";

SUBDESIGN tristate_buffer
(

IN1, IN2, En1, En2 :INPUT;
OUT1, OUT2 :BIDIR;
)

VARIABLE

OUT1_TNODE, OUT2_TNODE :TRI_STATE_NODE;

BEGIN

OUT1_TNODE = TRI(IN1, En1);
OUT1 = OUT1_TNODE;

OUT2_TNODE = TRI(IN2, En2);
OUT2 = OUT2_TNODE;

END;
```

#### Current Status of the TCM

- Read Module ID Code "3195"
- Read Module Serial Number
- Read Daughter Serial Number
- CAN Micro controller Reset
- Can Read Link Status
- Read two other registers


#### Current Status of the TCM

- Write to DPM
- Read from DPM
- "Hex display" display's Address
- "Hex display" display's Data
- LED's Display correct Data + Address
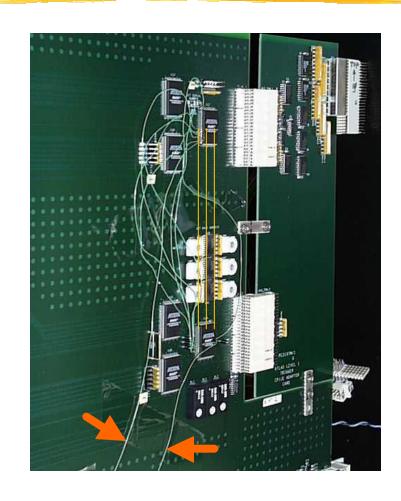
#### Current Status of the TCM

- Things to be checked
  - TTC Distribution (PECL)
  - CAN bus operations

- Do we need to make these modifications?
- Yes, but only two of them (link status)
- Use three enable signals for address decoding and eliminate 7 wire modifications.



Or, we could make the boards again taking into account the required modifications but keeping the original(ish) CPLD design.

- Change CPLD Design
- Keep and use boards already made(7) £2534 PCB only
- New boards will have more recourses, allowing for expansion of design

- Modify Boards
- Don't spend time modifying CPLD design
- Easier to debug
- Using design to full extent and as it was originally intended

- Recommendations
- Redesign the CPLD's
- 6 boards only need wire 2 modifications
- New boards with modifications increasing recourses if necessary

